

SET A

Name:	
Enrolment No:	

UNIVERSITY OF PETROLEUM AND ENERGY STUDIES
End Semester Examination, December 2018


Programme Name: B.Tech. CHE R&P, APE spe GS, APE spe US, ME	Semester : I
Course Name : Basic Electronics Engg.	Time : 03 hrs
Course Code : ECEG 1002	Max. Marks : 100
Nos. of page(s) : 2	



Instructions: 1) Mention Roll No at the appropriate place in the question paper. 2) Answers should be brief and concise. 3) Assume any missing data

SECTION A (20 marks)
All question of section A are compulsory

S. No.	Question	Marks	CO
Q 1	Enumerate the characteristics of a Zener diode. How a Zener diode is different from a crystal diode?	4	CO1
Q 2	Explain the physical structure of NPN transistor. Also label various majority charge carriers for the terminals.	4	CO1
Q 3	Explain the significance of digital logic. Why digital logic is preferred in design of computers?	4	CO1
Q 4	Explain the hexadecimal number system. Enumerate with the help of an example.	4	CO1
Q 5	What is meant by the term universal gate? Which gates are considered as universal gates? Explain with the help of an example.	4	CO1

SECTION B (40 marks)

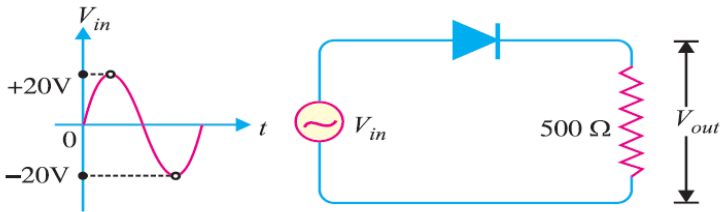Q 6	<p>An a.c. voltage of peak value 20V is connected in series with a silicon diode and load resistance of 500Ω. If the forward resistance of the diode is 10Ω, find: (i) Peak current through diode, and (ii) Peak output voltage. Also calculate the values if the diode is assumed to be an ideal diode.</p> <div style="text-align: center;">  </div> <p style="text-align: center;">Fig 1. Q5 – Diode circuit</p>	10	CO2
Q 7	Design a circuit for emitter bias based transistor configuration. Derive the expression for I_C, V_{CE} .	10	CO2
Q 8	Convert the following numbers into corresponding number system (3 marks each) A. $(60)_{10} = (?)_{16}$	10	CO2

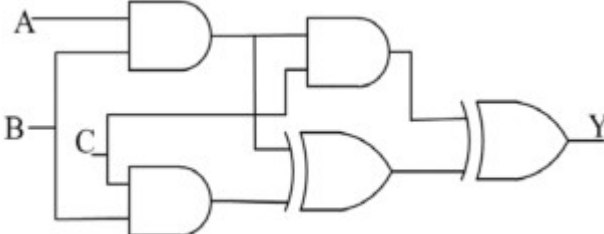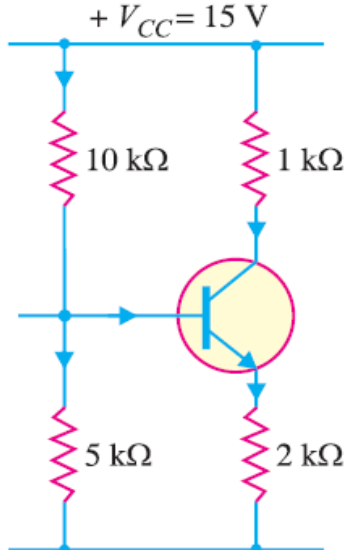	<p>B. $(001010110010100)_2 = (?)_{16}$</p> <p>C. $(171)_8 = (?)_2$</p> <p>D. $(1A4)_{16} = (?)_2$</p>		
Q 9	<p>Simplify the following Boolean expressions:</p> <p>A. $Y = (A+B+C) \cdot (A+B)$</p> <p>B. $Y = AB + ABC + ABC'$</p>	10	CO2
SECTION-C (25 marks)			
Q 10	<p>A. Derive the expression for current amplification factor (α) and base current amplification factor (β). In a transistor configuration, $I_B = 68 \mu A$, $I_E = 30 mA$, and $\beta = 440$. Determine the α rating the transistor. Also calculate the collector current.</p> <p>B. Develop the simplified Boolean expression for the following digital circuit:</p> 	10+10	CO3
Q 11	<p>A. For the following amplifier determine the operating point.</p> 	10+10	CO3
	<p>B. Develop a full adder using two half adders. Support your circuit with the help of a truth table.</p>		

Name:	
Enrolment No:	

UNIVERSITY OF PETROLEUM AND ENERGY STUDIES

End Semester Examination, December 2018

Programme Name: B.Tech. CHE R&P, APE spe GS, APE spe US, ME

Semester : I

Course Name : Basic Electronics Engg.

Time : 03 hrs

Course Code : ECEG 1002

Max. Marks : 100

Nos. of page(s) : 2


Instructions: 1) Mention Roll No at the appropriate place in the question paper. 2) Answers should be brief and concise. 3) Assume any missing data

SECTION A (20 marks)

All question of section A are compulsory

S. No.		Marks	CO
Q 1	Enumerate the characteristics of a crystal diode. Does a crystal diode obeys ohm's law?	4	CO1
Q 2	Explain the physical structure of PNP transistor. Also label various majority charge carriers for the terminals.	4	CO1
Q 3	Explain the significance of amplification. Which electronic devices are commonly used as amplifiers?	4	CO1
Q 4	Explain the binary number system. Enumerate with the help of an example.	4	CO1
Q 5	Why NAND gate is considered as a universal gate? Explain with the help of an example.	4	CO1

SECTION B (40 marks)

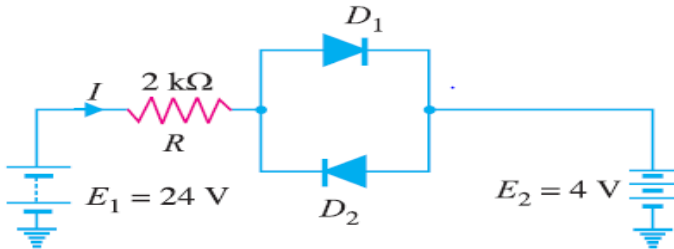Q 6	Determine the current I in the circuit shown in figure 1. Assume the diodes to be of silicon and forward resistance of the diodes to be zero.		10	CO2
Fig1. Q5 – Diode circuit				
Q 7	Design a circuit for voltage divider based transistor configuration. Derive the expression for I_C, V_{CE} .	10	CO2	
Q 8	Simplify the following Boolean expressions: A. $Y = 1 + A(B \cdot \dot{C} + BC + \dot{B} \cdot \dot{C}) + A\dot{B}C + AC$ B. $Y = (A + \dot{B} + \dot{C}) + (B + \dot{C})$	10	CO2	
Q 9	Convert the following numbers into corresponding number system (3 marks each) A. $(40)_{10} = (?)_{16}$	10	CO2	


- B. $(000111101100)_2 = (?)_{16}$
 C. $(152)_8 = (?)_2$
 D. $(C4)_{16} = (?)_2$

SECTION-C (40 marks)

Q 10

A. For a transistor derive the expression for α and β . In a transistor configuration, $I_B = 18 \mu A$, $I_E = 25 mA$, and $\alpha = 0.096$. Determine the β rating the transistor. Also calculate the collector current.

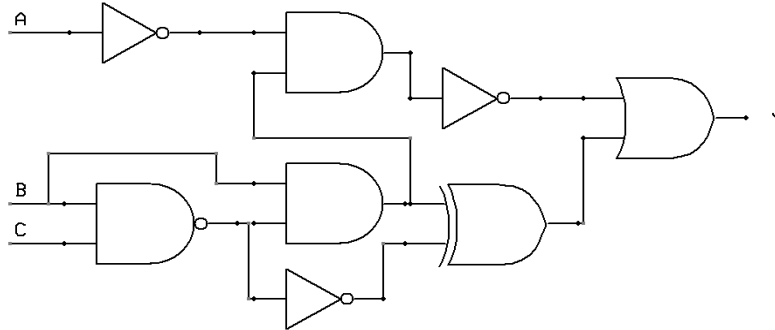B. Develop the simplified Boolean expression for the following digital circuit:



10+10

CO3

Q 11

A. Design an emitter bias amplifier such to satisfy the following requirements:

$+V_{CC} = 15 V$, $-V_{EE} = 15 V$, $R_B = 100 K\Omega$, $R_E = 10 K\Omega$, $R_C = 4.7 K\Omega$, $\beta = 110$

Also calculate the operating point for the amplifier.

B. Develop a full adder using two half adders. Support your circuit with the help of a truth table.

10+10

CO3