

Name:

Enrolment No:



UNIVERSITY OF PETROLEUM AND ENERGY STUDIES

End Semester Examination, May 2019

Programme Name: BT-EL

Course Name : Linear Integrated Circuits

Course Code : ECEG 2008

Nos. of page(s) :02

Semester : IV

Time : 02 hrs

Max. Marks : 100

Instructions:

All questions are compulsory.

SECTION A

S. No.		Marks	CO
Q1.	<p>Determine V_{out} for the two connections shown in below Figure 1. Assume $V_1 = 5V$, $V_a = 1V$ and $V_b = 2V$.</p> <p>(a)</p> <p>(b)</p> <p>Figure 1</p>	5	CO2
Q2.	<p>Discuss why Schmitt trigger is also known as square wave generator.</p>	5	CO1
Q3.	<p>With neat block diagram, explain the operation of 8-bit successive approximation register type ADC. What is the maximum conversion time for this type of ADC.</p>	5	CO2

Q4.	Write short notes on virtual ground concept.	5	CO1
SECTION B			
Q5.	Show that the High pass RC network performs filtering and op-amp provides amplification?	10	CO2
Q6.	<p>A regenerative comparator (Schmitt Trigger) circuit is shown in Figure 2.</p> <p>Derive expressions for upper threshold and lower threshold voltages, V_{UT} and V_{LT} respectively and hence the value of hysteresis voltage V_H. Calculate V_{UT}, V_{LT}, V_H for the given values of $R_1 = 54 \text{ k}\Omega$ and $R_2 = 2 \text{ k}\Omega$.</p>	10	CO3
Figure 2			
Q7.	<p>A sine wave with 4 V peak-to-peak amplitude and 2 kHz frequency is applied at the input of the circuit. Plot the input and output waveforms. $V_{cc} = +15 \text{ V}$</p>	10	CO3
Figure 3			
Q8.	<p>A circuit whose output does not have any stable state and the Output has two Quasi-Stable states using op-amp to produce a square wave output where output keeps on changing its own from 1state to another state and Vice Versa. Design the circuit for above mentioned specifications.</p>	10	CO3

SECTION-C			
Q9	<p>An astable multivibrator flashes the electric bulb such that its ON time will be 5 seconds and off time will be 3 seconds. Design the circuit diagram for the above mentioned specifications calculating:</p> <ul style="list-style-type: none"> • Values for R_A and R_B. <p>Assuming the value of capacitance in μF.</p>	20	CO4
Q10	<p>Design a timer, which should turn ON heater immediately after pressing a push button and should hold heater in 'ON-state' for 10 seconds.</p>	20	CO4

Name:

Enrolment No:



UNIVERSITY OF PETROLEUM AND ENERGY STUDIES

End Semester Examination, May 2019

Programme Name: BT-EL

Course Name : Linear Integrated Circuits

Course Code : ECEG 2008

Nos. of page(s) :02

Semester : IV

Time : 02 hrs

Max. Marks : 100

Instructions:

All questions are compulsory.

SECTION A

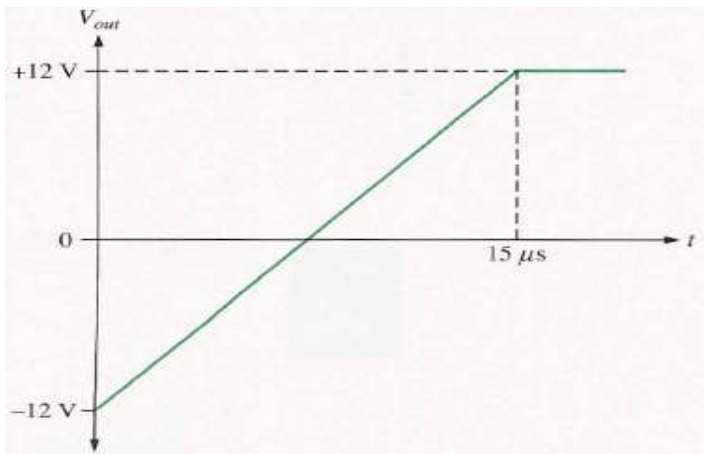
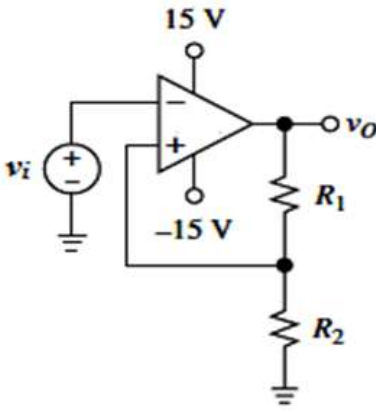
S. No.		Marks	CO
Q1.	A 555 timer is configured to run in astable mode with $R_A = 4k\Omega$, $R_B = 4k\Omega$ and $C=0.01\mu F$. Determine the frequency of the output and duty cycle.	5	CO2
Q2.	Discuss why Astable Multivibrator is also known as square wave generator.	5	CO1
Q3.	An op-amp has dc gain of 10^4 and a gain of 500 at a frequency of 1kHz. Calculate its break frequency and UGB (Unity Gain Bandwidth).	5	CO2
Q4.	Figure 1 shows the output voltage of an op-amp in response to the step input. Find the slew rate. 	5	CO1

Figure 1

SECTION B

Q5.	With neat block diagram, explain the operation of 8-bit successive approximation register type ADC.	10	CO3
Q6.	A regenerative comparator (Schmitt Trigger) circuit is shown in Figure 2	10	CO3

	<p>Derive expressions for upper threshold and lower threshold voltages, V_{UT} and V_{LT} respectively and hence the value of hysteresis voltage V_H. Calculate V_{UT}, V_{LT}, V_H for the given values of $R_1 = 54 \text{ k}\Omega$ and $R_2 = 4 \text{ k}\Omega$.</p> <div style="text-align: center;">  </div> <p style="text-align: center;">Figure 2</p>		
Q7.	Design a RC phase shift FET oscillators defining condition for sustained oscillations.	10	CO3
Q8.	Design a circuit using op-amp to produce a square wave whose output has one stable state and one quasi-stable state where circuit generates pulse output if trigger input is applied.	10	CO3
SECTION-C			
Q9	<p>Design a circuit diagram of an astable multivibrator to generate the output signal with frequency of 1kHz and the duty cycle of 75%. The design process should have</p> <ul style="list-style-type: none"> (i) Well labelled waveforms (ii) Value of R_A & R_B. <p>Assuming the value of capacitance in μF.</p>	20	CO4
Q10	Design a 555 timer based square wave generator to produce a symmetrical square wave of 1kHz. If $V_{cc} = 12\text{V}$, draw the voltage across timing capacitor and the output.	20	CO4