

| | |
|---------------|--|
| Name: |  |
| Enrolment No: | |


UNIVERSITY OF PETROLEUM AND ENERGY STUDIES


End Semester Examination, Dec 2021


Programme Name: B.Tech ECE
Course Name: Analog Electronics I.
Course Code: ECEG 2011
Nos. of page(s): 4

Semester: III
Time: 03 hrs
Max. Marks: 100

| | | | |
|--------|---|--------------|------------|
| S. No. | SECTION A : (4X5 = 20 M) Attempt all the questions | Marks | COs |
|--------|---|--------------|------------|
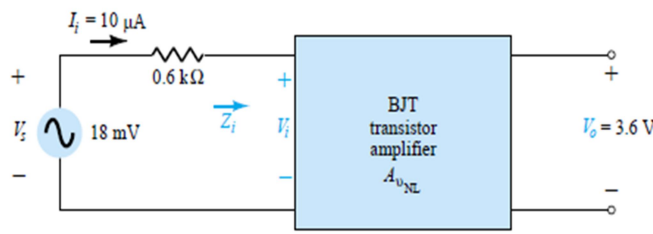
| | | | |
|-----|---|---|-----|
| Q 1 | <p>For a given the BJT configuration as shown in Fig 1 below, determine: (a) V_i. (b) Z_i. (c) A_{VNL} (d) A_{vs}.</p> <div style="text-align: center;">  </div> <p style="text-align: center;">Fig1</p> | 4 | CO1 |
|-----|---|---|-----|
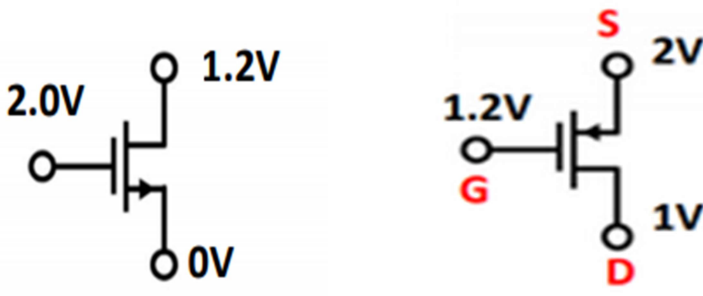
| | | | |
|-----|--|---|-----|
| Q 2 | <p>Determine the operating region for the given MOSFET configurations as shown in fig 2?</p> <div style="text-align: center;">  </div> <p style="text-align: center;">Fig. 2</p> | 4 | CO2 |
|-----|--|---|-----|
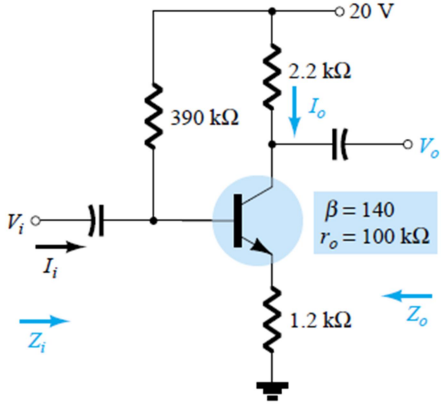
| | | | |
|--|---|----|-----|
| Q 3 | Sketch the equivalent hybrid model for CE npn BJT and mention all the hybrid model parameters. | 4 | CO1 |
| Q4 | Explain the pinch off condition in JFETs and its impact over the drain current. Sketch the N channel JFET with proper regions? | 4 | CO2 |
| Q5 | Mention the impact of cascade network of amplifiers on the overall gain and the bandwidth of the amplifier. Explain by considering the frequency response? | 4 | CO4 |
| SECTION B : (4X10 = 40M) | | | |
| Attempt All the questions | | | |
| Q 6 | Sketch the curve of $I_D = 0.5 \cdot 10^{-3} (V_{GS})^2$ and $I_D = 0.5 \cdot 10^{-3} (V_{GS} - 4)^2$ for V_{GS} from 0 to 10 V. Does $V_T = 4$ V have a significant impact on the level of I_D for this region? | 10 | CO2 |
| Q7 | <p>(a) Determine the operating point of the given amplifier as shown in Fig 3 under DC analysis? Evaluate the following performance parameters of the given CE amplifier below</p> <p>(b) Find Z_i and Z_o.</p> <p>(c) Calculate A_v and A_i.</p> | 10 | C03 |
|  | | | |
| Fig 3 | | | |
| Q8 | <p>(a) Analyze the Characteristics of Enhancement type and Depletion type MOSFET?</p> <p>(b) Draw the transfer and output characteristics of N- channel JFET and elaborate on the input impedance of the JFET?</p> <p style="text-align: center;">OR</p> <p>Compute the Gate capacitance C_G, gate to drain capacitance C_{GD}, gate to source capacitance for the Fig. 4. Consider the overlapping capacitances $C_{GSO} = C_{GDO} = 5$ fF/m². What will be effects on these capacitances when horizontal dimension are scaled by 1/4 and vertical dimensions by 1/3.</p> | 10 | CO2 |

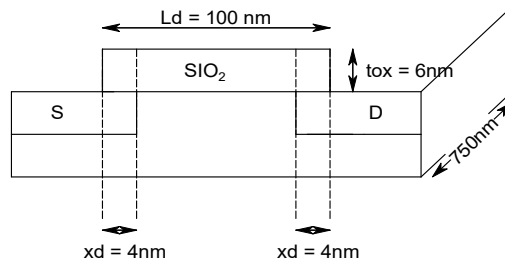


Fig. 4

Q9 Determine the value of resistance R in the below circuit (Fig. 5) for the 180 nm technology where $W/L = 4$ and gate oxide capacitance formed by dielectric = $20 \mu\text{F}/\text{m}^2$ oxide thickness (electron mobility = $1200 \text{ cm}^2/\text{Vs}$)?

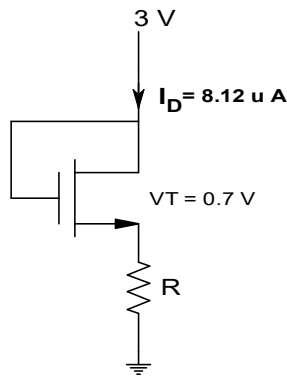


Fig. 5


10

C03

SECTION-C (2x20=40 M)

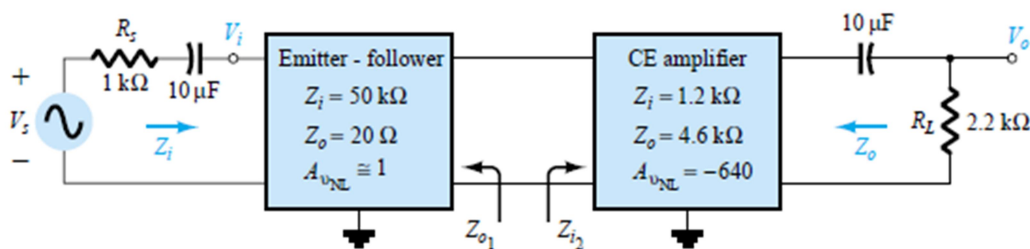Q10 Consider the BJT amplifier shown below (Fig. 6) and determine the followings:

- Calculate Z_i and Z_o .
- Find Over all A_v and A_i .
- Calculate the output for $V_i = 250\text{m} \cdot \sin 2\pi 100t$.
- Draw the Gain Frquency spectrum of the given amplifier.



20

CO4

Fig. 6

Q11

The fixed-bias common source configuration having an operating point defined by $V_{GS_Q} = 2 \text{ V}$ and $I_{D_Q} = 5.625 \text{ mA}$, with $I_{D_{SS}} = 10 \text{ mA}$ and $V_{GS_{OFF}} = -8 \text{ V}$. The network configuration is shown in Fig. 7 with an applied input signal V_i . The value of Y_o is provided as $50 \mu\text{S}$.

- (a) Determine g_m .
- (b) Find r_d .
- (c) Determine Z_i .
- (d) Calculate Z_o .
- (e) Determine the voltage gain A_v .

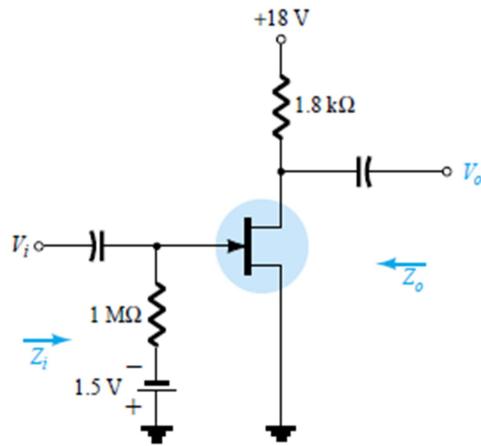


Fig. 7

OR

- (a) Explain why it is important to set the Q point at the middle of the DC load line. Draw the proper DC load line on output characteristics for common emitter configuration
- (b) Describe the thermal run away condition in BJTs and how it affects the operating point of an amplifier.

20

CO3