

Name:

Enrolment No:



UNIVERSITY OF PETROLEUM AND ENERGY STUDIES
End Semester Examination, December 2022

Course: Analog Electronics-I
Program: B. Tech (ECE)
Course Code: ECEG2011

Semester: III
Time: 03 hrs.
Max. Marks: 100


Instructions: The QP is 3 pages long. Draw the neat and clean diagram wherever it is needed.

SECTION A

S. No.		Marks	CO
Q 1	Given that $\beta_{dc} = 120$ and $I_C = 2.0$ mA, find I_E and I_B .	4	CO1
Q 2	State Miller's theorem with the aid of a circuit diagram. Write the importance of this theorem in circuit analysis.	4	CO1
Q 3	Calculate the power gain in decibels for each of the following cases. (a) $P_o = 100$ W, $P_i = 5$ W. (b) $P_o = 100$ mW, $P_i = 5$ mW.	4	CO3
Q 4	For a typical BJT ($h_{ie} = 2.4$ k, $h_{fe} = 100$, $h_{re} = 4 \times 10^{-4}$, and $h_{oe} = 25$ μ S), sketch the following: a. Common-emitter hybrid equivalent model. b. Common-emitter r_e equivalent model.	4	CO1
Q 5	A n-channel JFET has device parameters of $I_{DSS} = 8$ mA and $V_P = 4$ V. Sketch the transfer characteristics.	4	CO2

SECTION B

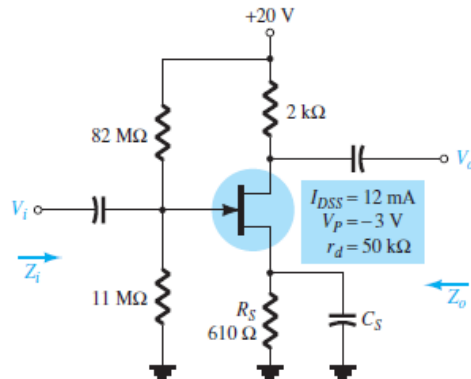
Q 6 Determine Z_i , Z_o , and V_o for the network of the following figure if $V_i = 20$ mV.



10


CO2

Q 7	Three identical cascaded stages have an overall upper 3-dB frequency of 20kHz and a lower 3-dB frequency of 20Hz. What are f_L and f_H of each stage? Assume non-interacting stages.	10	CO4
Q 8	(a) Compare Field Effect Transistors' (FET) advantages and disadvantages to those of BJTs. (b) Draw the basic construction of a depletion-type MOSFET. What is the effect of V_{GS} on channel width?	5+5	CO2
Q 9	Given that $I_{CQ} = 2 \text{ mA}$ and $V_{CEQ} = 10 \text{ V}$ determine R_1 and R_C for the network of following figure	10	CO1

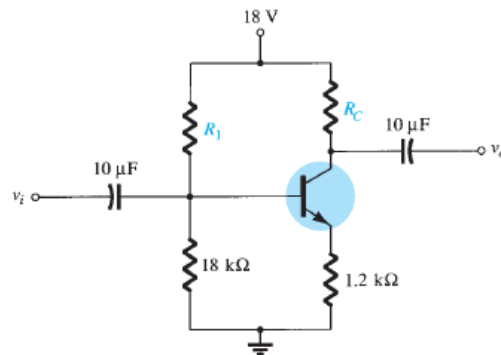


SECTION-C

Q 10	(a) What is the significant difference between the construction of an enhancement type MOSFET and a depletion type MOSFET. (b) For the n-channel depletion-type MOSFET of below figure, determine: (i) I_{DQ} and V_{GSQ} (ii) V_{DS}	5+15	CO2
------	---	------	-----

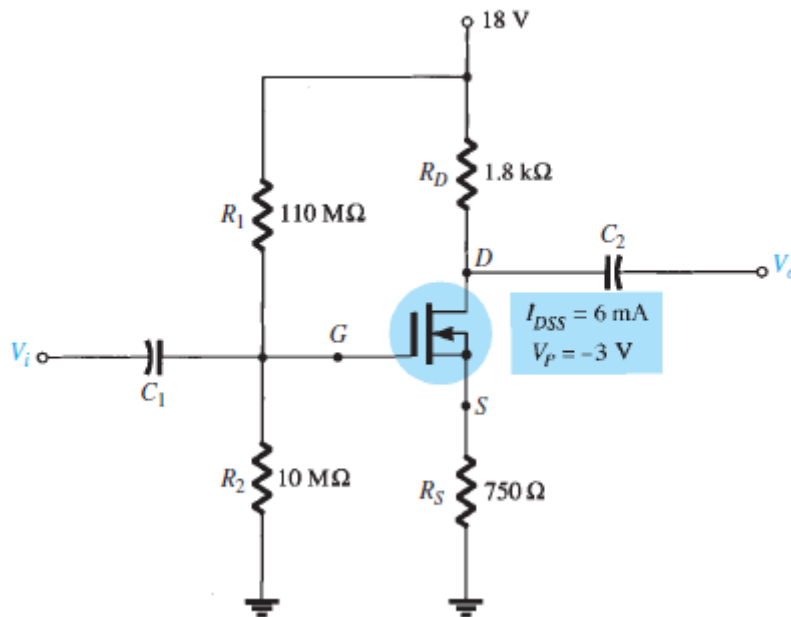

Q 11	Determine Z_i , Z_o , and V_o for the network of following figure if $V_i = 20 \text{ mV}$.	20	CO3
------	--	----	-----

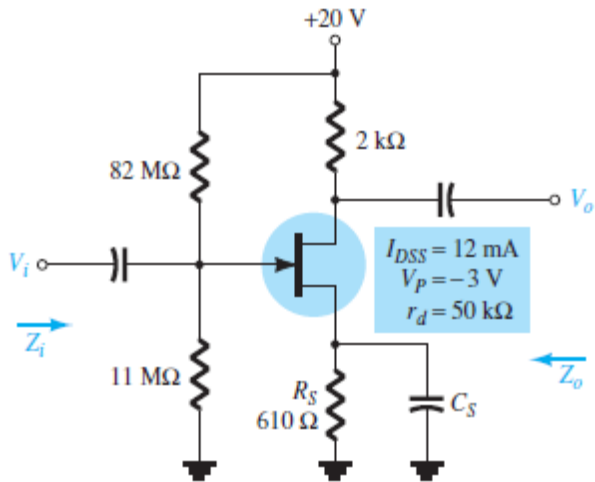

OR

For the Darlington network of the following figure:

- Determine the dc levels of V_{B1} , V_{C1} , V_{E2} , V_{CB1} , and V_{CE2} .
- Find the currents I_{B1} , I_{B2} , and I_{E2} .
- Calculate Z_i and Z_o .
- Determine the voltage gain $A_v = V_o / V_i$ and current gain $A_i = I_o / I_i$.

