

Name:	
Enrolment No:	

**UNIVERSITY OF PETROLEUM AND ENERGY STUDIES**  
**End Semester Examination, December 2022**

**Course:Digital System Design**

**Semester: III**

**Program: B.Tech Electronics and Communication**

**Time : 03 hrs.**

**Course Code: ECEG2037**

**Max. Marks: 100**

**Instructions:**

**SECTION A**  
**(5Qx4M=20Marks)**


S. No.		Marks	CO
Q 1	A transmitter uses a single error-correcting code for the message using even parity. The message received at the receiving end is 1110101. Check and correct the error	4	<b>CO1</b>
2	Minimize the following logic function using K-Map $Y(A,B,C,D)=\sum m(0,1,2,3,5,7,8,9,11,14)$	4	<b>CO2</b>
3	Implement the following expression using a single 8:1 multiplexer $Y(A,B,C,D)=\sum m(0,2,3,6,8,9,12,14)$	4	<b>CO3</b>
4	Draw the logic circuit of J-K flipflop using D flipflop.	4	<b>CO2/CO 4</b>
5	Explain a bidirectional shift register	4	<b>CO2/CO 4</b>

**SECTION B**  
**(4Qx10M= 40 Marks)**

Q 6	Simplify the following Boolean function : $Y(A,B,C,D,E)=\sum m(0,1,2,3,16,17,18,19)$	10	<b>CO2</b>
7	Design a MOD-12 synchronous counter using T flipflop	10	<b>CO2/CO 4</b>
8	a)Design a two-input TTL NAND gate totempole output with capacitive load b)Explain active and passive pull up	10	<b>CO5</b>
9	a)Design CMOS three input NAND and NOR gate. b)What are the characteristics of CMOS? Define Fan in and Fan out.	10	<b>CO5</b>

**SECTION-C**  
**(2Qx20M=40 Marks)**

Q 10	a)What do you understand by Moore and Mealy circuit?Design a sequential circuit using J-K flipflops for the state diagram shown below:	20	<b>CO3/CO 4</b>
------	--	----	-----------------

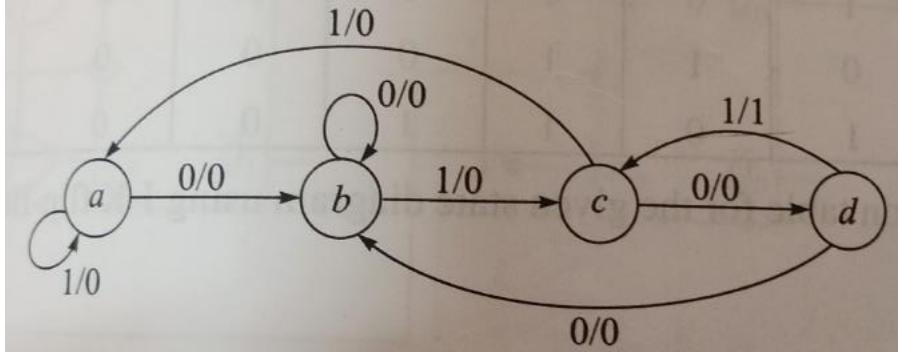

b) Design a mod 9 ripple counter using T flipflop

Q11	a) Design a circuit to generate the sequence 0-2-5-4-7 avoiding the lock out condition by using J-K flipflop b) Design a sequence generator to generate the sequence 11001011	<b>20</b>	<b>CO3/CO 4</b>
-----	---	-----------	---------------------