

Name:

Enrolment No:



UPES

End Semester Examination, Dec 2024

Programme Name: MSc Physics

Semester: I

Course Name: Analog Electronics

Time: 03 hrs

Course Code: ECEG7034

Max. Marks: 100

Nos. of page(s):2

Instructions: [a] A scientific calculator is allowed. [b] Symbols have their usual meanings

SECTION A

Answer all questions

S.No.		Marks	CO
Q 1	Derive the expression for the intrinsic carrier concentration ( $n_i$ ) in a semiconductor.	5	CO1
Q 2	For a reverse-biased P-N junction, derive the expression for junction capacitance ( $C_j$ ) and explain how it varies with the applied reverse voltage.	5	CO2
Q 3	A silicon P-N junction diode has a reverse saturation current of $I_s = 10^{-12} A$ at 300K. Calculate the forward current when the diode is forward-biased with a voltage of 0.7 V. (Use $kT/q=0.0259V$ ).	5	CO3
Q 4	What is Op-Amp. Briefly describe the five practical applications of Op-Amps in the electronics industry.	5	CO4

SECTION B

Answer all questions (Q 5 has an internal choice)

Q 5	In a silicon sample at 300 K, the electron mobility $\mu_n$ is $1350 \text{ cm}^2/\text{V-s}$ , and the hole mobility $\mu_p$ is $480 \text{ cm}^2/\text{V-s}$ . An electric field $E$ of $1000 \text{ V/cm}$ is applied across the sample. Calculate the drift current density $J_{\text{drift}}$ if the electron concentration $n=10^{16} \text{ cm}^{-3}$ and the hole concentration $p=10^{15} \text{ cm}^{-3}$ .  <b>OR</b> Derive the Einstein relation (relationship between diffusion coefficient and mobility) for a semiconductor.	10	CO1
Q 6	Sketch the I-V characteristics of an LED. Explain how LEDs emit light, and describe one application of LEDs in optoelectronics.	10	CO2
Q7	Explain the purpose of adding an emitter resistor $R_E$ in a common-emitter amplifier circuit. How does the emitter resistor contribute to the stability of the amplifier's operating point?	10	CO3
Q8	An ideal Op-Amp integrator has a feedback capacitor, $C=1\mu\text{F}$ and an input resistor, $R=100\text{k}\Omega$ . If a constant input voltage $V_{\text{in}}=1\text{V}$ is applied, find the output voltage $V_{\text{out}}$ as a function of time.	10	CO4

**SECTION C**

**Answer any one question (Question 10 has an internal choice)**

Q 9	What is FET? What are the differences between FET and BJT? Give the construction and working of n channel JFET with a proper diagram. Explain the output characteristics and transfer characteristics of n-channel JFET.	<b>2+5+7 +6</b>	<b>CO3</b>
Q 10	[a] What is feedback? Explain the negative feedback with a diagram. Derive the expression of its voltage gain. [b] An inverting amplifier circuit is built with an operational amplifier, where the input resistor $R_{in} = 5k\Omega$ and the feedback resistor $R_f = 50k\Omega$ . If the input voltage $V_{in} = 0.5V$ , calculate the output voltage $V_{out}$ . Assume an ideal op-amp. <p style="text-align: center;">OR</p> [a] Explain how an Op-Amp works as an integrator. Provide an example of a real-world application [b] Derive the Barkhausen criterion for oscillation and explain why it is necessary for oscillator circuits	<b>10+10</b>	<b>CO4</b>