

Name:

Enrolment No:



UPES

End Semester Examination, December 2024

Programme Name: B. Tech (Electronics & Communication Engineering) / Electronics & Computer Engineering)

Course Name : VLSI Design

Time : 03 Hrs

Course Code : ECEG-3049

Max. Marks : 100

Nos. of page(s) : 02

Semester : V

Instructions: Assume any data in programming, if required.

SECTION A (4 x 5 = 20 Marks)

Attempt all the questions

S. No.		Marks	CO
Q.1	Discuss the ASIC Design Flow in detail and detail the different abstraction levels in ICs with example.	5	CO1
Q.2	Realize the output of the logic diagram shown in Fig. 1	5	CO3
Q.3	What are the different styles of modeling followed in VHDL based design. Design a full adder using data flow and behavioral model.	5	CO4
Q.4	Draw the logic diagram and functional table to support common cathode display of the 7-segment display (0 to 9) and develop the code in VHDL programming language to support the same functionality.	5	CO5

 
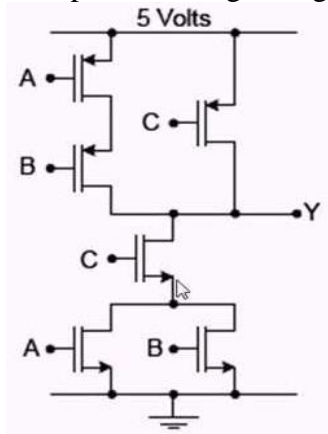


Fig. 1 CMOS Realization

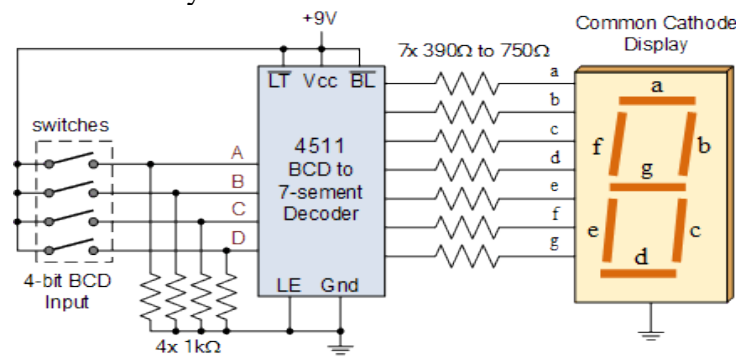


Fig.2 Common Cathode -7 Segment Display

SECTION B (4 x 10 = 40 Marks)

Attempt all the questions

Q.5	(a) Explain the concept of propagation delay and Noise Margin with examples in MOSFET circuits. (b) Realize the following functions using NMOS and CMOS. $Y = \overline{A \cdot (B + CD)}$ $Y = \overline{\overline{X} + Y + Z}$	10	CO2
Q.6	What is the significance of stick diagram and layout diagram for understanding MOSFET design? Draw the stick diagram and layout design of 2 input NAND and XOR gate based on CMOS logic. <p align="center">OR</p> Detail the fabrication process of nnpn-BJT transistor.	10	CO3
Q.7	Detail the functionality of enhancement type NMOS/PMOS under different regions. Explain the drain voltage characteristics and transfer characteristics in detail	10	CO1
Q.8	Draw the voltage transfer curve for the NMOS/CMOS inverter and derive the mathematical expression to estimate the value of V_{OH} , V_{OL} , V_{IL} and V_{IH} for NMOS/CMOS inverter circuit and detail the functionality.	10	CO2

SECTION-C (2 x 20 = 40 Marks)

Attempt any two the followings

Q.9	(a) Draw the cross-sectional view of CMOS. Detail all the steps and fabrication process of CMOS using P-Well Process. (b) Draw the FPGA design flow used for synthesis the logic. Draw the architecture of any one of the FPGA and explain the functionality: XC 3000, SPARTAN 6, Virtex 7.	10+10	CO3
Q.10	(a) Consider a process technology for which $L_{min} = 0.4 \mu m$, $t_{ox} = 8 \text{ nm}$, $\mu_n = 450 \text{ cm}^2/\text{V-s}$ and $V_t = 0.7 \text{ V}$ (i) Find C_{ox} and K'_n (ii) For a MOSFET with $W/L = 8 \mu m/0.8 \mu m$, Calculate the value of V_{GS} and V_{DSmin} needed to operate the transistor in the saturation region with a dc current $I_D = 100 \mu A$. (iii) For the same device, find the value of V_{GS} required to cause the device to operate as a 1000Ω resistor for very small V_{DS} . (b) Derive the mathematical equation of PMOS/NMOS for saturation and active regions.	10+10	CO4
Q.11	(a) Design the chip using VHDL/ Verilog HDL that supports the following behaviour. <div data-bbox="479 1575 1015 1837" data-label="Diagram"> </div> (b) Draw the structure of CPLD (Max Altera 7000) and explain the functionality. Compare the CPLD with FPGA.	10+10	CO5